

Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023

Date: 16-08-2023

Name: K. Haripriya	SRN: PES2UG22CS243	Section: D
--------------------	--------------------	------------

Week# ____1____

Program Number: ____1____

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT AND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

I. Verilog Code Screenshot

```
and2.v
1  module basic_and(a, b, y);
2  input a, b;
3  output y;
4  assign y = a & b;
5  endmodule
6
7
```


II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>iverilog -o test1 and2.v and_tb.v

C:\iverilog\bin>vvp test1
VCD info: dumpfile and2_test.vcd opened for output.
      0a=0, b=0, y=0
      5a=0, b=1, y=0
     15a=1, b=0, y=0
     30a=1, b=1, y=1

C:\iverilog\bin>gtkwave and2_test.vcd
```

III. GTKWAVE Screenshot

 

IV. Output Table to be completed and included

a	b	y
0	0	0
0	1	0
1	0	0
1	1	1

Date: 16-08-2023

Name: K. Haripriya	SRN: PES2UG22CS243	Section: D
--------------------	--------------------	------------

Week# ____1____

Program Number: ____2____

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT OR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE OR GATE TRUTH TABLE

I. Verilog Code Screenshot

```
2_or.v
1  module basic_or(a, b, y);
2  input a, b;
3  output y;
4  assign y = a | b;
5  endmodule
```


II. Verilog VVP Output Screen Shot

```
^C
C:\iverilog\bin>iverilog -o test2 2_or.v 2_or_tb.v

C:\iverilog\bin>vvp test2
VCD info: dumpfile or_test.vcd opened for output.
      0a=0, b=0, y=0
      5a=0, b=1, y=1
     15a=1, b=0, y=1
     30a=1, b=1, y=1

C:\iverilog\bin>gtkwave or_test.vcd
```

III. GTKWAVE Screenshot

 

IV. Output Table to be completed and included

a	b	y
0	0	0
0	1	1
1	0	1
1	1	1

Date: 16-08-2023

Name: K. Haripriya	SRN: PES2UG22CS243	Section: D
--------------------	--------------------	------------

Week# 1

Program Number: 3

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A NOT GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOT GATE TRUTH TABLE

I. Verilog Code Screenshot

```
1 module basic_not(a, y);
2   input a;
3   output y;
4   assign y = ! a;
5   endmodule
```

II.

III. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>iverilog -o test3 3_not.v 3_not_tb.v

C:\iverilog\bin>vvp test 3
test: Unable to open input file.


C:\iverilog\bin>vvp test3
VCD info: dumpfile not_test.vcd opened for output.
          0a=0, y=1
          5a=1, y=0

C:\iverilog\bin>gtkwave not_test.vcd

GTKWave Analyzer v3.3.100 (w)1999-2019 BSI

[0] start time.
[5] end time.
```

IV. GTKWAVE Screenshot

 

V. Output Table to be completed and included

a	y
0	1
1	0

Date: 16-08-2023

Name: K. Haripriya	SRN: PES2UG22CS243	Section: D
--------------------	--------------------	------------

Week# ____1____

Program Number: ____4____

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NAND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NAND GATE TRUTH TABLE


I. Verilog Code Screenshot

```
1 module basic_nand(a, b, y);  
2 input a, b;  
3 output y;  
4 assign y = !(a & b);  
5 endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>iverilog -o test4 4_nand.v 4_nand_tb.v  
  
C:\iverilog\bin>vvp test4  
VCD info: dumpfile nand_test.vcd opened for output.  
          0a=0, b=0, y=1  
          5a=0, b=1, y=1  
         15a=1, b=0, y=1  
         30a=1, b=1, y=0  
  
C:\iverilog\bin>gtkwave nand_test.vcd
```

III. GTKWAVE Screenshot

 

IV. Output Table to be completed and included

a	b	y
0	0	1
0	1	1
1	0	1
1	1	0

Date: 16-08-2023

Name: K. Haripriya	SRN: PES2UG22CS243	Section: D
--------------------	--------------------	------------

Week# ____1____

Program Number: ____5____

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOR GATE TRUTH TABLE


I. Verilog Code Screenshot

```
1 module basic_nor(a, b, y);  
2   input a, b;  
3   output y;  
4   assign y =! (a | b);  
5   endmodule  
6
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>iverilog -o test5 5_nor.v 5_nor_tb.v  
  
C:\iverilog\bin>vvp test5  
VCD info: dumpfile nor_test.vcd opened for output.  
          0a=0, b=0, y=1  
          5a=0, b=1, y=0  
         15a=1, b=0, y=0  
         30a=1, b=1, y=0  
  
C:\iverilog\bin>gtkwave nor_test.vcd
```

III. GTKWAVE Screenshot

 

IV. Output Table to be completed and included

a	b	y
0	0	1
0	1	0
1	0	0
1	1	0

Date: 16-08-2023

Name: K. Haripriya	SRN: PES2UG22CS243	Section: D
--------------------	--------------------	------------

Week# 1 Program Number: 6

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE


I. Verilog Code Screenshot

```
1 module basic_xor(a, b, y);  
2   input a, b;  
3   output y;  
4   assign y = a ^ b;  
5 endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>iverilog -o test6 6_xor.v 6_xor_tb.v  
  
C:\iverilog\bin>vvp test6  
VCD info: dumpfile xor_test.vcd opened for output.  
      0a=0, b=0, y=0  
      5a=0, b=1, y=1  
     15a=1, b=0, y=1  
     30a=1, b=1, y=0  
  
C:\iverilog\bin>gtkwave xor_test.vcd
```

III. GTKWAVE Screenshot

 

IV. Output Table to be completed and included

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

Date: 16-08-2023

Name: K. Haripriya	SRN: PES2UG22CS243	Section: D
--------------------	--------------------	------------

Week# 1 Program Number: 7

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XNOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE


I. Verilog Code Screenshot

```
module basic_xnor(a, b, y);  
  input a, b;  
  output y;  
  assign y = ! (a ^ b);  
endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>iverilog -o test7 7_xnor.v 7_xnor_tb.v  
  
C:\iverilog\bin>vvp test7  
VCD info: dumpfile xnor_test.vcd opened for output.  
          0a=0, b=0, y=1  
          5a=0, b=1, y=0  
         15a=1, b=0, y=0  
         30a=1, b=1, y=1  
  
C:\iverilog\bin>gtkwave xnor_test.vcd
```

III. GTKWAVE Screenshot

 

IV. Output Table to be completed and included

a	b	y
0	0	1
0	1	0
1	0	0
1	1	1

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature:

Name:

SRN:

Section: D

Date: 16-08-2023

